

TMS320C6201 Power Supply

APPLICATION REPORT: SPRA447

David Bell

*Digital Signal Processing Solutions
April 1998*



IMPORTANT NOTICE

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain application using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

TRADEMARKS

TI is a trademark of Texas Instruments Incorporated.

Other brands and names are the property of their respective owners.

CONTACT INFORMATION

US TMS320 HOTLINE	(281) 274-2320
US TMS320 FAX	(281) 274-2324
US TMS320 BBS	(281) 274-2323
US TMS320 email	dsph@ti.com

Contents

Abstract.....	7
Product Support	8
World Wide Web.....	8
Email	8
Design Problem	9
Solution	9
References.....	12

Figures

Figure 1. Power Supply Circuit for 'C6201	10
Figure 2. Fail-Safe Power Supply Circuit	12

Tables

Table 1. VID[4:0] Codes for Regulated Voltage Levels.....	11
---	----

TMS320C6201 Power Supply

Abstract

This document describes how to provide power to the Texas Instruments (TI™) TMS320C6201 digital signal processor (DSP). The TMS320C6201 DSP is a 3.3V I/O device with an internal core voltage level of 2.5V for rev 1 or 2 (1.8V for rev 3). To provide power to this device, separate supplies must be used for each of the two voltages and proper power sequencing to the device must be provided.



Product Support

World Wide Web

Our World Wide Web site at **www.ti.com** contains the most up to date product information, revisions, and additions. Users registering with TI&ME can build custom information pages and receive new product updates automatically via email.

Email

For technical issues or clarification on switching products, please send a detailed email to **dsph@ti.com**. Questions receive prompt attention and are usually answered within one business day.



Design Problem

How do I provide power to the TMS320C6201?

Solution

The TMS320C6201 DSP is a 3.3V I/O device with an internal core voltage level of 2.5V for rev 1 or 2 (1.8V for rev 3). To provide power to this device, separate supplies must be used for each of the two voltages and proper power sequencing to the device must be provided.


For power-up sequencing, ramp up the core (CVdd) supply first. Then ramp up the 3.3V I/O (DVdd) supply. For power-down sequencing, remove DVdd, then CVdd. The order is not mandatory but, if the DVdd must be brought up first, ensure that the 3.3V supply does not exceed the 2.5V by more than 2V, and the power up should take less than 25ms.

The reasoning behind the power sequencing is that essentially no harm will come to the device if the core is powered up and the I/O is not. There simply will be no input or output capability. If the I/O is powered up and the core is not, however, the transistors in the buffer/drivers will be driven while in an unknown state.

If this sequencing is not possible, it is permissible to ramp up both the supplies concurrently, provided that precautions are taken. The DVdd must not exceed the CVdd by more than 2V. Both power supplies should achieve 95% of their voltage level within a 25ms window. The 2.5V supply should be able to handle an output current of 3A (maximum consumption by the rev 2 device).

The simplest way to provide dual power to the DSP is to split a single source to two linear voltage regulator circuits (one regulating 3.3V and the other 2.5V). A sample circuit is shown in Figure 1 for a 5V source, using two 4A adjustable linear regulators from Cherry Semiconductor (part #CS-5204-1). Since the two regulated voltages are derived from the same source, power up sequencing should not be a problem. For component selection criteria, see the Cherry SC data sheet.

Figure 1. Power Supply Circuit for 'C6201¹

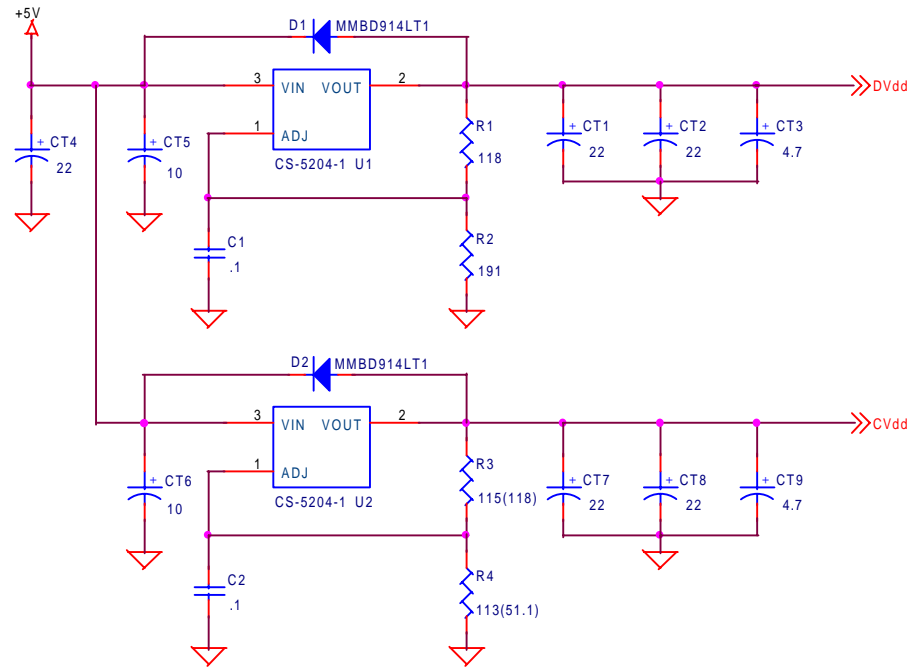

The regulated voltage levels provided by the circuits shown in Figure 1 are determined by the resistor values. The output of each regulator is governed by the equation:

$$V_{OUT} = V_{REF} \times \left(\frac{R1 + R2}{R1} \right) + I_{Adj} \times R2$$

where V_{REF} is the voltage drop across $R1$ (1.25V fixed), and I_{Adj} is the current from the ADJ pin (typically 50µA).

If linear regulators are used in a system, large heat sinks will be required. This may make the design impractical, depending on the application.

A better, though more complicated solution, uses discrete regulators. Discrete regulators both emit a smaller amount of heat and can provide a fail-safe design.

¹ Numbers in parentheses indicate values used in a 1.8V core voltage design. If linear regulators are used, they need to be connected to large heat sinks.



To provide fail-safe operation of the device, power should be supplied so that if the core supply fails during operation, the I/O supply will be shut down as well. This can be accomplished using regulators having a “Power Good” output, whereby the device has a logical output indicating whether or not its regulated output is correct, and an “Inhibit” input, by which the device may be shut down by an external signal. The “Power Good” signal of the core supply should be tied directly to the “Inhibit” pin of the I/O supply. This configuration ensures that both power supplies will turn off if the core fails. In addition, an improper voltage level will not damage the device, and unknown outputs will not be driven from the device to the system. Figure 2 shows an example of this type of circuit using two Fairchild RC5050² discrete voltage regulators.

Pins VID[4:0] of the regulator program the voltage level of the output. Table 1 lists the required pin connections for voltage levels of 3.3V, 2.5V, and 1.8V. For a complete list of possible voltage levels, see the Raytheon data sheet. In a design based on a ‘C6201 with a 2.5V core, VID[4:0] should be brought out to jumpers to allow forward compatibility. In this way, a 1.8V core device could be used in its place at a later time. The VID[4:0] pins for the 3.3V I/O may be hard-wired, as this voltage level will not change.

Table 1. VID[4:0] Codes³ for Regulated Voltage Levels


Voltage Level	VID4	VID3	VID2	VID1	VID0
3.3	1	0	0	1	0
2.5	1	1	0	1	0
1.8	0	0	1	0	1

For detailed information on component selection for a design with the RC5050, please see the Fairchild data sheet.

² Similar devices are available from Elantec (#EL7571C and #EL7560C).

³ 0 indicates that the pin is shorted to ground. 1 indicates that the pin is left unconnected.

Figure 2. Fail-Safe Power Supply Circuit

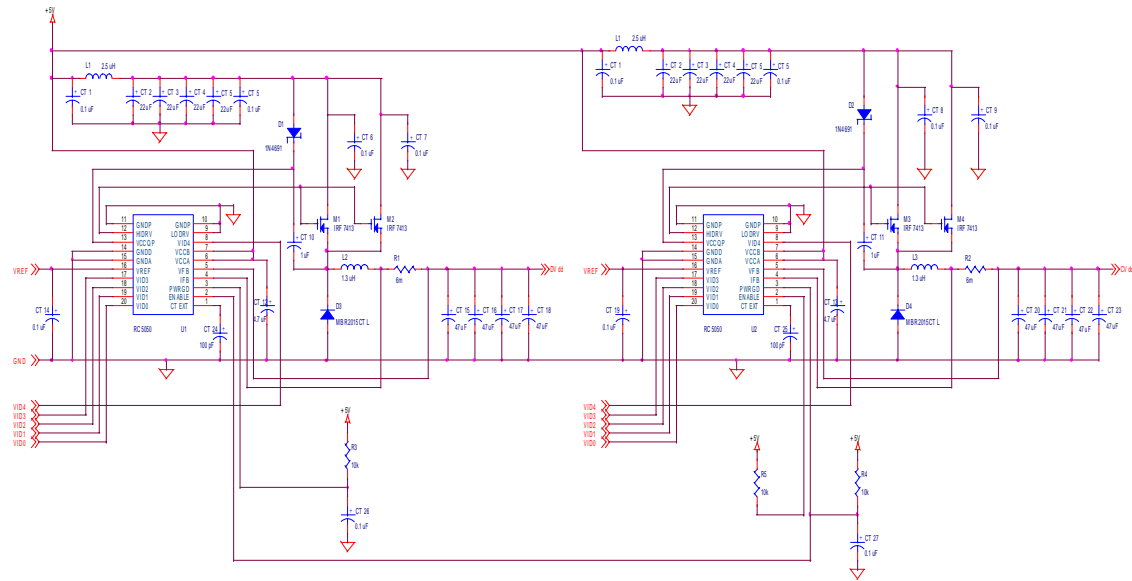

References

RC5050 Programmable DC-DC Converter for Low Voltage
Microprocessors Data Sheet, Fairchild
http://www.fairchildsemi.com/cf/sales_contacts/

CS-5204-1 4A Adjustable, and 3.3V and 5V Fixed Linear Regulators
Data Sheet, Cherry Semiconductor
<http://www.cherrysemiconductor.com>